

4 (**short**) Using Thevenin's theorem, or otherwise, calculate the current through the 6 V battery in Fig. 4.

[10]

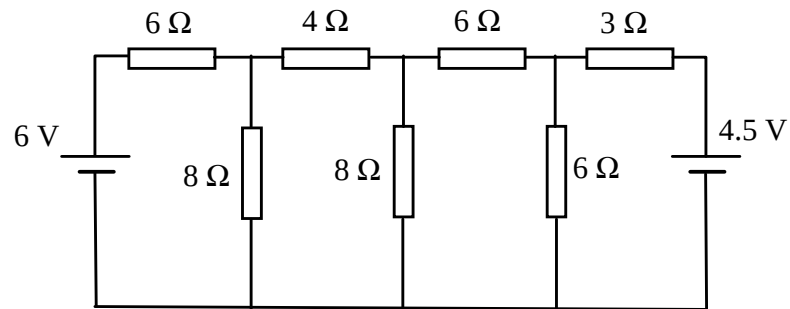


Fig. 4