

5 (**short**) Using Thévenin's theorem or otherwise, determine the current flowing in the  $2\ \Omega$  resistor in the circuit of Fig. 5. [10]

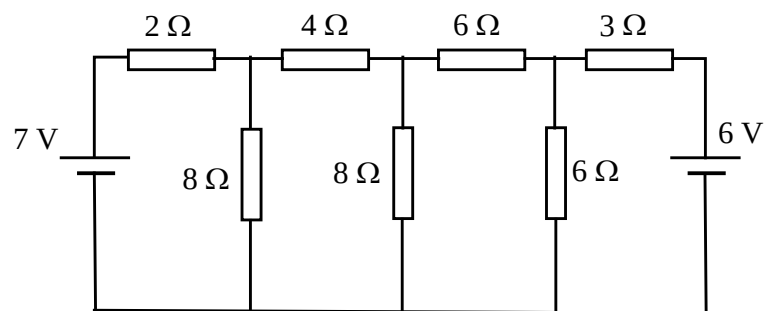


Fig. 5