

7 (short)

- (a) Draw a circuit showing how an SR bistable can be constructed by means of only 2-input NAND gates. Write Boolean expressions relating the outputs and inputs of the bistable. [2]
- (b) Describe the features of a JK bistable that are not present in an SR bistable and discuss in what ways these are advantageous. [4]
- (c) In an SR bistable the inputs S and R have values $S = R = 1$ and these then change to $S = R = 0$. Explain how the outputs of the bistable would behave. [4]