

3 (**short**) Figure 3 shows a radio frequency tuned circuit connected to a 200 kHz, 50 V (rms) RF power output. Determine the complex impedance of the circuit and hence find the magnitude and phase of the input current with respect to the voltage source. [10]

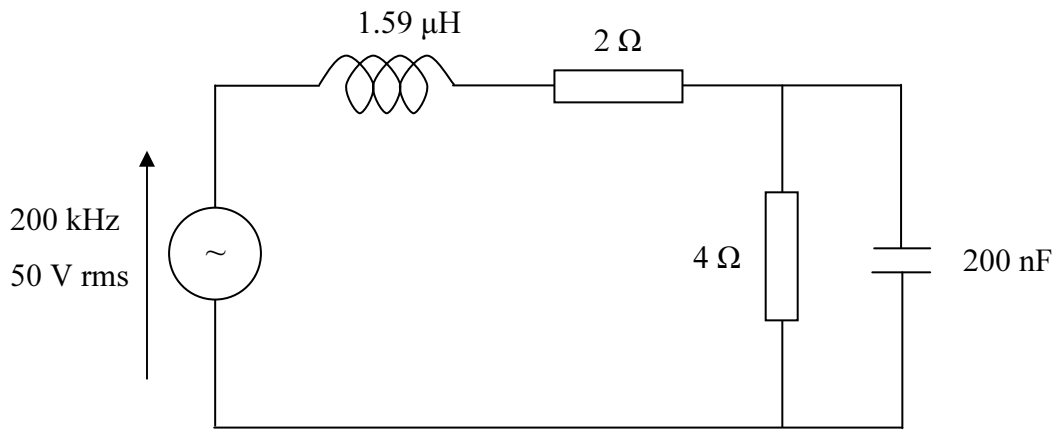


Fig. 3