

SECTION B

6 (short) The characteristics of NMOS transistors M1 and M2 are shown in Fig. 7(a).

(a) Using the characteristics provided, briefly explain the function of the NMOS transistor M2 in Fig. 7(b). *A copy of Fig. 7(a) is reproduced at the end of this paper for you to detach and hand in with your answer.* [5]

(b) What is the logic implemented by the circuit in Fig. 7(b)? Explain the drawback of this circuit. [5]

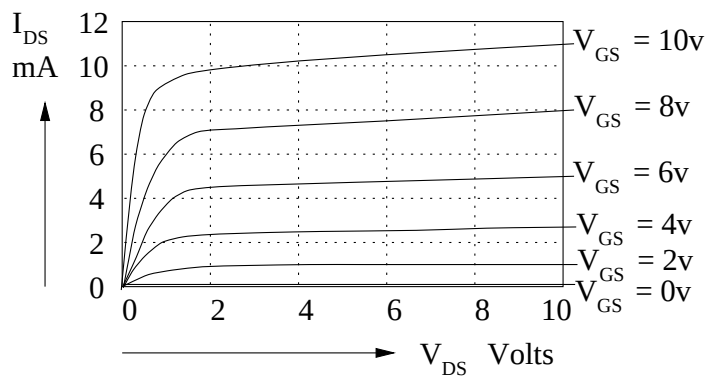


Fig. 7 (a)

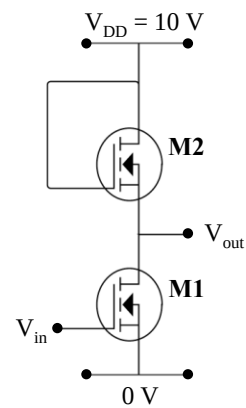


Fig. 7 (b)