

Section A

1 **(short)** Using star-delta transformation, determine the current flowing in the resistor R_1 between nodes A and B. [10]

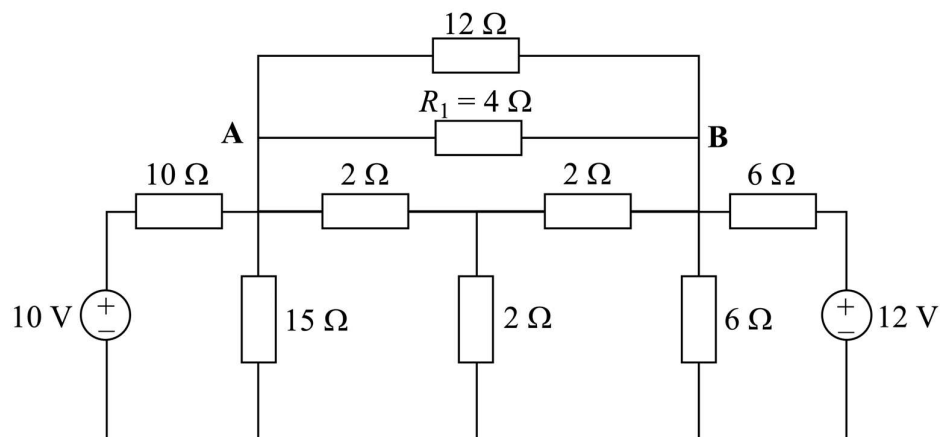


Fig. 1