

2 **(short)** Calculate the total complex impedance of the circuit shown in Fig. 2. Find the magnitude and phase of the supply current with respect to the 230 V, 50 Hz voltage source.

[10]

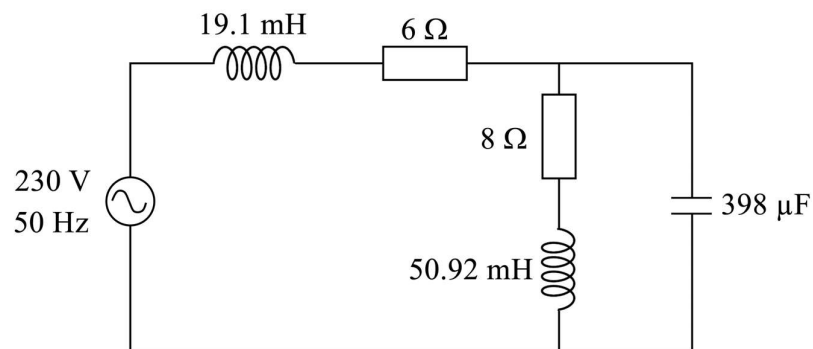


Fig. 2