

SECTION B

6 (short)

- (a) Explain what is meant by static 0 and static 1 hazards in combinational digital circuits. [2]
- (b) A function F is defined as $F = \bar{A} \cdot \bar{C} + A \cdot D$. Determine the potential hazards and recommend solutions for these hazards. [8]