

Section A

- 1 (short) Using Thevenin's and/or Norton's theorem, simplify the circuit in Fig. 1 and derive the expression for current in the resistor **R**. [10]

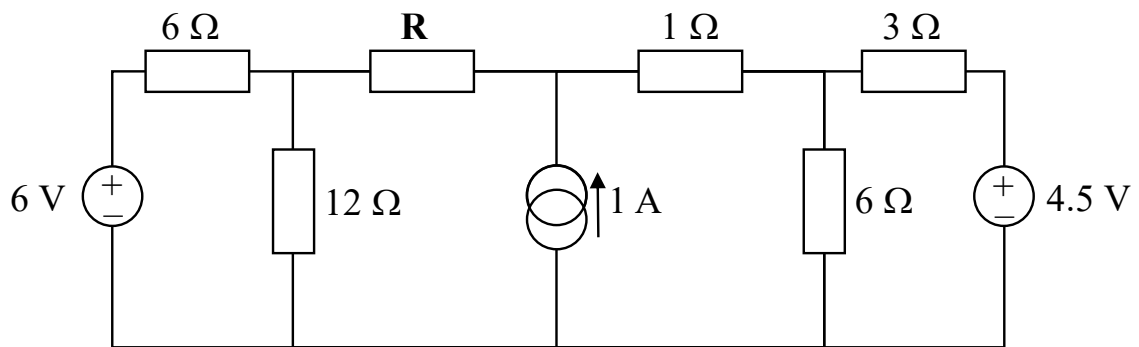


Fig. 1