

- 2 (short) Calculate the total complex impedance of the circuit shown in Fig. 2. Find the magnitude and phase of the supply current i . [10]

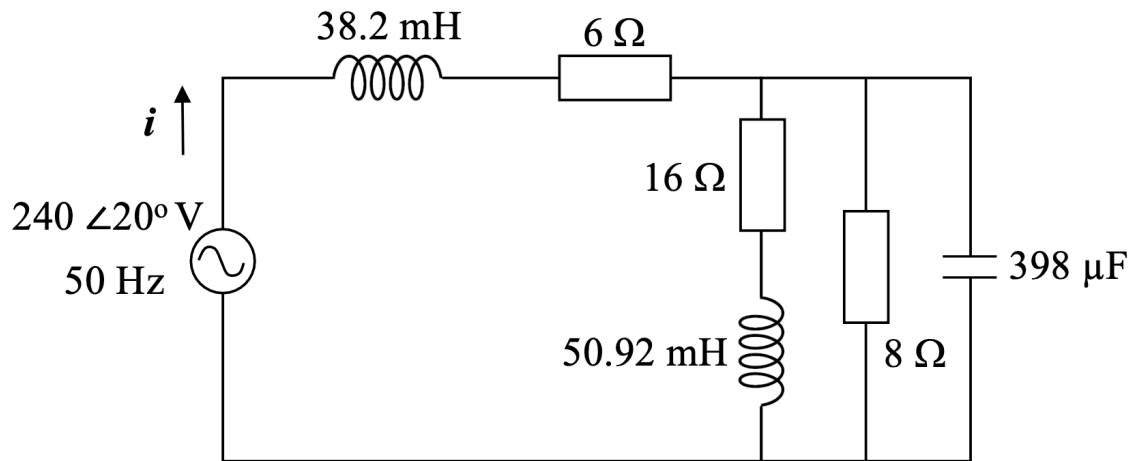


Fig. 2