

Section A

- 1 **(short)** Figure 1 shows an ac bridge circuit with an ac source of frequency ω . Find the frequency at balance in terms of R_3 and C . [10]

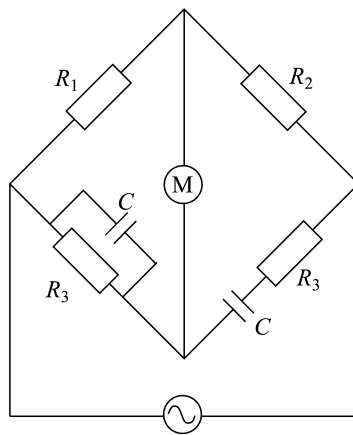


Fig. 1