

- 2     **(short)** Calculate the current drawn from the 120 V rms supply if the supply frequency is 50 Hz in Fig. 2. What is the resonant frequency of this circuit? [10]

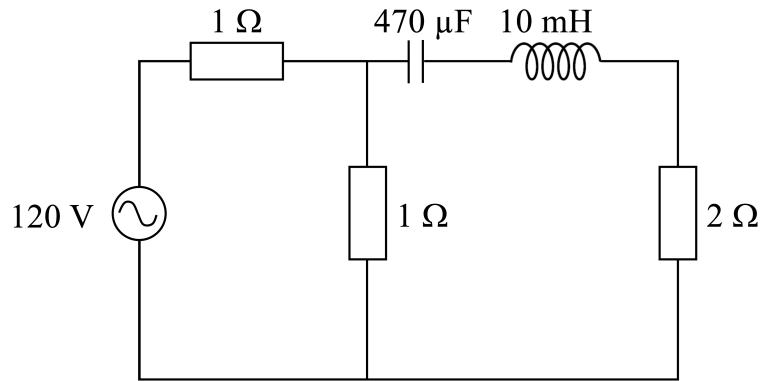


Fig. 2